



How to Connect an Electric Circuit

Step 1: Get your equipment You will need:


- a battery,
- two wires,
- a bulb,
- and a switch.

Step 2: Connect the battery to the bulb Connect one wire from the battery to the metal part at the bottom of the bulb.

Step 3: Connect the bulb to the switch Use another wire to join the bulb to the switch.

Step 4: Complete the circuit Join the switch back to the battery with another wire.

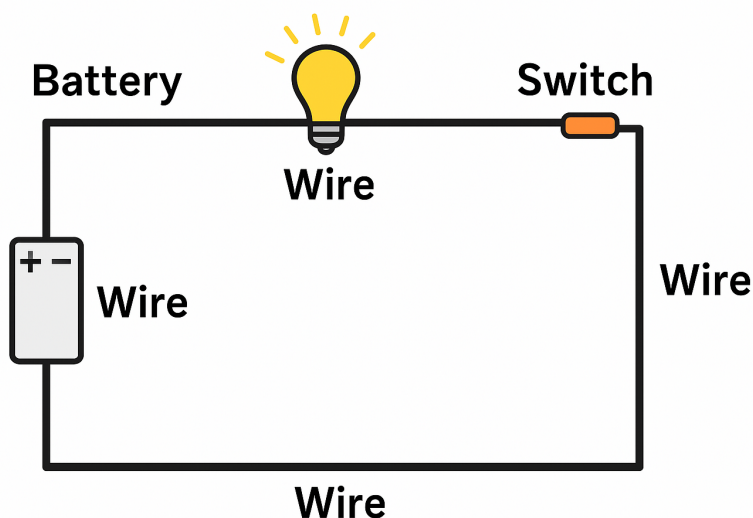Step 5: Press the switch When you press the switch, the circuit will close, and the bulb should light up.



Questions

1. What are the four things you need for a simple circuit?

👉 To make a simple circuit, you need...

2. Where do you connect the first wire?

👉 The first wire goes from...

3. What does a switch do in a circuit?

👉 A switch in a circuit...

4. What must happen for the bulb to light up?

👉 For the bulb to light up, the circuit must...

5. Why might a bulb not light up even if the wires are connected?

👉 A bulb might not light up because...